Score Along Dashed Lines – – – – – – –

Cut Along Dotted Lines ....

BC548 Transistor

To negative lead of
battery connector

E   C

B

470Ω resistor

LED 1

Mini photocell

LED 2

To positive lead of
battery connector

1KΩ resistor   50 K trimpot